

DE ANZA COLEGE – PHYSICS 4B LAB – FALL 2024

Lab 5 – Resistors in Series and in Parallel

TITLE

Resistors in Series and in Parallel

OBJECTIVE


To analyze properties of resistors connected in series and in parallel

THEORY

Resistors in Series

Resistors connected in series have an equivalent resistance of:

$$R_{eq} = R_1 + R_2$$

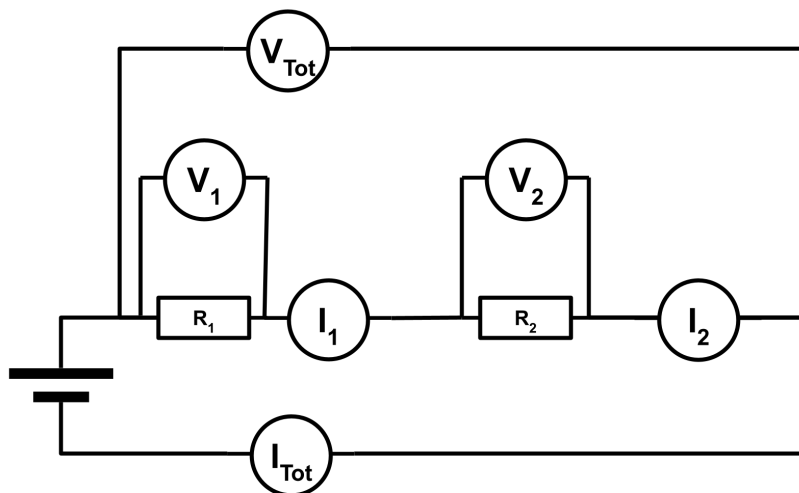


In this case

$$R_{eq} = V_{tot}/I_{tot}$$

Resistors in Parallel

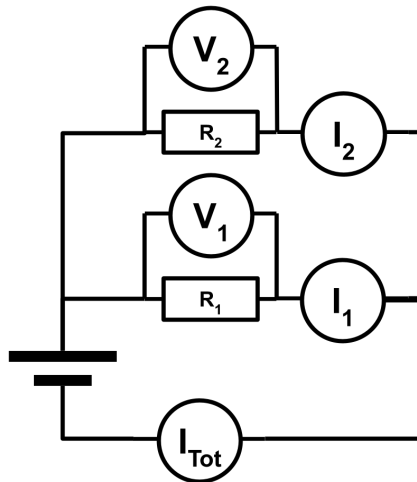Resistors connected in parallel have an equivalent resistance given by:



$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Here the following will be true:

$$V_{\text{tot}} = V_1 = V_2$$

and

$$I_{\text{tot}} = I_1 + I_2.$$

Therefore we would have

$$R_{\text{eq}} = V_{\text{tot}}/I_{\text{tot}}.$$


APPARATUS

1. HP-DMM (used as an ammeter)
2. Hand-held DMM (used as a voltmeter)
3. Power Supply
4. 2 different resistors less than $5\text{K } \Omega$
5. Circuit boards
6. Leads and alligator clips


PROCEDURE

Part 1 Measuring R_{eq}

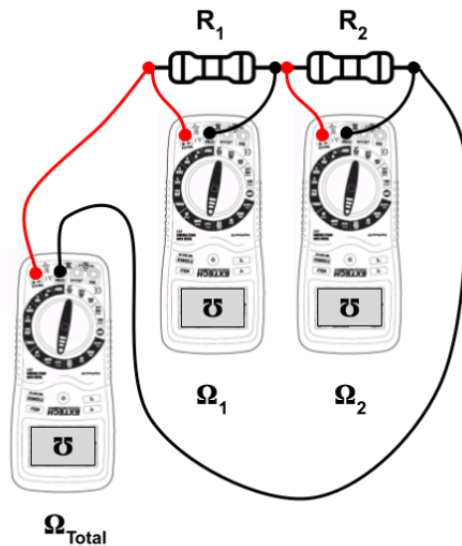1. Measure R_1 and R_2 with the DMM.
2. Connect R_1 and R_2 in series, using the circuit board, and measure R_{eq} with the DMM. Compare R_{eq} with the expected value of $R_{\text{eq}} = R_1 + R_2$.





3. Connect R_1 and R_2 in parallel, using the circuit board, and measure R_{eq} with the DMM. Compare $1/R_{\text{eq}}$ with the expected value of $1/R_{\text{eq}} = 1/R_1 + 1/R_2$.

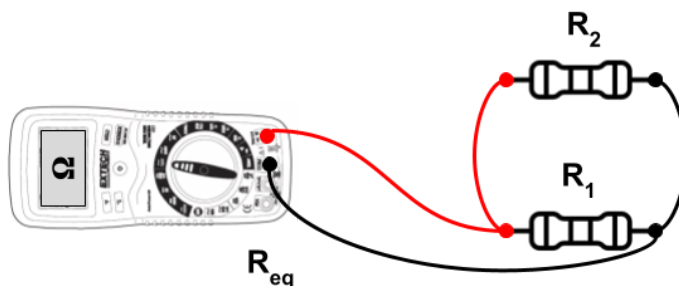

Part 1: Series Combination

1. Connect R_1 and R_2 in series and apply a voltage of $\approx 10V$ with power supply.
2. Measure the total current in the circuit and compare with expected value of $I_{\text{expected}} = V/R_{\text{eq}}$, where $R_{\text{eq}} = R_1 + R_2$.
3. Measure V_1 and V_2 and show that $V = V_1 + V_2$.
4. Calculate $I_1 = V_1/R_1$ and $I_2 = V_2/R_2$ and show that $I_1 = I_2 = I$.

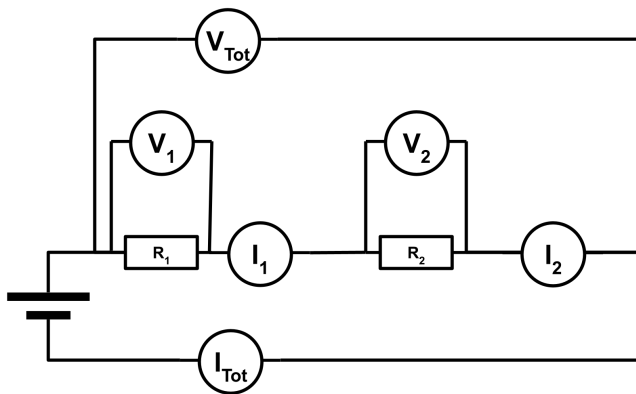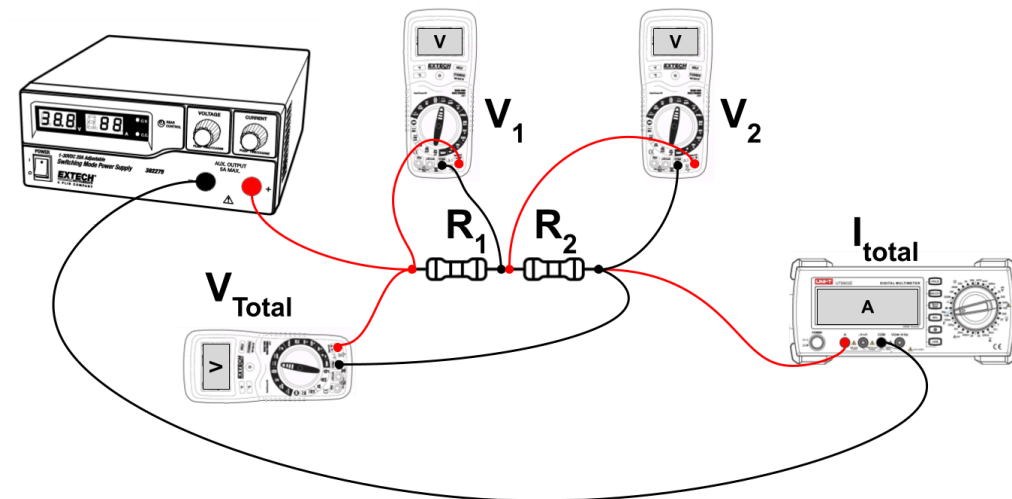

Part 2: Parallel Combination

1. Connect R_1 and R_2 in parallel and apply the same voltage as in the series combination.
2. Measure the total current in the circuit and compare with the expected value of $I_{\text{expected}} = V/R_{\text{eq}}$, where $1/R_{\text{eq}} = 1/R_1 + 1/R_2$
3. Measure I_1 and I_2 and show that $I_1 + I_2 = I_{\text{measured}}$
4. Measure V_1 and V_2 and show that $V_1 = V_2 = V$.
5. Calculate $I_1 = V_1/R_1$ and $I_2 = V_2/R_2$ and show that $I_1 + I_2 = I_{\text{expected}}$.
6. Compare $I_1 = V_1/R_1$ and $I_2 = V_2/R_2$ with measured values.

